

Name:

I Honor Code:

KEY

Instructions:


- Complete the 6 problems in the allotted time, and *report your answers in the box provided on this page.*
- Use the space on the accompanying pages to work the problems. Do not use a bluebook. Attach additional worksheets if necessary.
- If you wish to have partial credit awarded for any of your incorrect answers **you must write clearly and legibly.** Explain your work in words, if necessary.
- Don't Panic.

Good Luck.

Problem	Answer	
10	i. B	vi. D
	ii. A	vii. D
	iii. C	viii. B
	iv. C	ix. D
	v. D	x. A
15	2	$V_{out} = \frac{R_1}{R_1+R_2} (V_1 - V_2 - V_3)$ Volts
15	3	$V_{out} = \frac{30}{29} V = 1.0345 V$
25	4	$V_{out} = (-1.4523 + j7.0540)V = 7.2020 \angle 101.6337^\circ V$
25	5	$P_V = -57.9235 W$ $P_{1mH} = 0 W$ $P_{10\Omega} = 28.343 W$ $P_{20\Omega} = 74.9993 W$ $P_{2mH} = 0 W$ $P_{10uF} = 0 W$ $P_{25A} = -15.1247 W$
	6	$R = 1000 \Omega$ $L = .01 H$


(10 Points) 1. Choose the best answer for each of the 10 multiple choice problems below

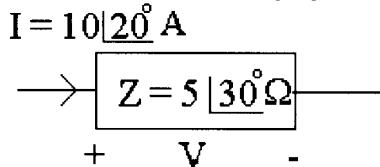i. The voltage, V, in the following figure is:




- a. $2\angle-10^\circ$ Volts
- b. $50\angle50^\circ$ Volts
- c. $5\angle10^\circ$ Volts
- d. $15\angle50^\circ$ Volts

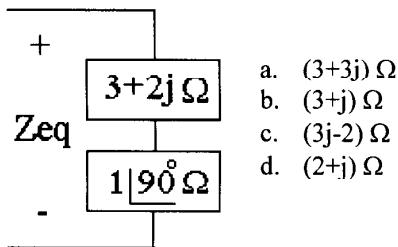ii. The equivalent impedance, Z_{eq} , is:



- a. $(3+3j)\Omega$
- b. $(3+j)\Omega$
- c. $(3j-2)\Omega$
- d. $(2+j)\Omega$

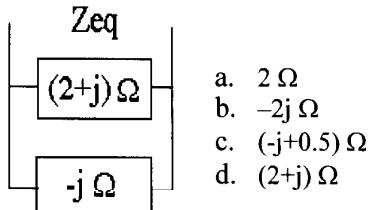iii. The equivalent impedance, Z_{eq} , is:



- a. 2Ω
- b. $-2j\Omega$
- c. $(-j+0.5)\Omega$
- d. $(2+j)\Omega$


iv. In rectangular form, $(1+j)/(2-j)$ is

- a. 3
- b. $(-0.2-0.6j)$
- c. $(0.2 + 0.6j)$
- d. $(3+j)$

v. In polar form, $(-1-j)$ is

- a. $1.414\angle45^\circ$
- b. $1\angle-135^\circ$
- c. $1 \angle 45^\circ$
- d. $1.414\angle-135^\circ$

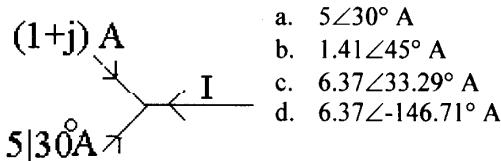vi. The current, I, in the following figure is:



vii. A certain element has $V=5$ Volts and $I=(2+3j)$ Amps. The impedance, Z , must be:

- a. $(0.4-0.6j)\Omega$
- b. $(10 - j15)\Omega$
- c. $(0.4 - 0.6j)\Omega$
- d. $(.7692 - j1.1538)\Omega$

viii. The element of vii above consists of a resistor and another component in series. The second component must be:

- a. a resistor
- b. a capacitor
- c. an inductor
- d. Cannot be determined.

ix. It is possible to construct an impedance of -3Ω using resistors, capacitors, and inductors alone.


- a. True
- b. False

x. Consider the figure of problem iii. The $-j\Omega$ impedance is just a capacitor. If $\omega=1000$ rad/sec, what is the capacitance, C?

- a. $1mF$
- b. $1000F$
- c. $1uF$
- d. Cannot be determined.

Q&A

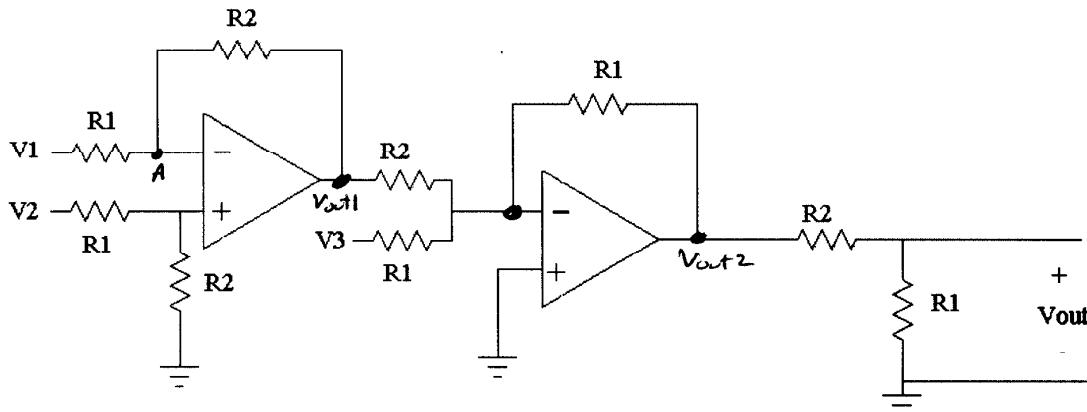2. (15 Points) Find V_{out} as a function of the inputs V_1 , V_2 , and V_3 in the following circuit.



1

2

$$\text{opamp 1: } \frac{A - V_1}{R_1} + \frac{A - V_{out1}}{R_2} = 0 \quad \text{or} \quad V_{out1} = A \left(\frac{R_2}{R_1} + 1 \right) - \frac{R_2}{R_1} V_1$$

$$\frac{A - V_2}{R_1} + \frac{A}{R_2} = 0 \quad A \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = V_2 / R_1$$

$$A = \left(\frac{R_1 R_2}{R_1 + R_2} \frac{V_2}{R_1} \right)$$

$$\begin{aligned} V_{out1} &= \frac{V_2}{R_1} \left(\frac{R_2 + R_1}{R_1} \right) \left(\frac{R_1 R_2}{R_1 + R_2} \frac{V_2}{R_1} \right) - \frac{R_2}{R_1} V_1 \\ &= \frac{R_2}{R_1} V_2 - \frac{R_2}{R_1} V_1 \quad \underline{V_{out1} = \frac{R_2}{R_1} (V_2 - V_1)} \end{aligned}$$

Opamp 2:


$$\frac{0 - V_{out1}}{R_2} + \frac{0 - V_3}{R_1} + \frac{0 - V_{out2}}{R_1} = 0$$

$$V_{out2} = -V_{out1} \left(\frac{R_1}{R_2} \right) - V_3$$

$$= \underline{V_1 - V_2 - V_3}$$

$$V_{out} = \frac{R_1}{R_1 + R_2} (V_1 - V_2 - V_3)$$

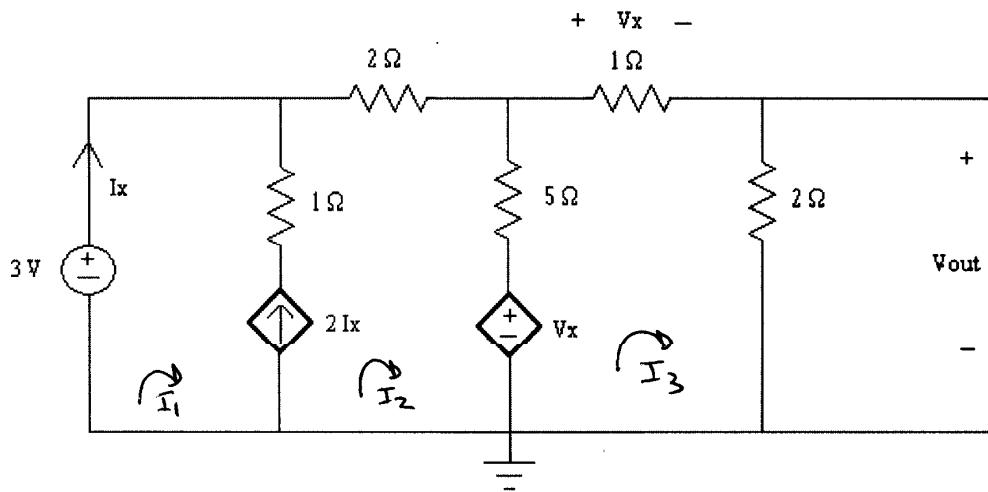3. (15 Points) Find V_{out} in the following circuit.



$$\text{loop 1: } -3 + 2I_2 + 5(I_2 - I_3) + V_x = 0$$

$$7I_2 - 5I_3 + V_x = 3 \quad V_x = I_3$$

$$\underline{7I_2 - 4I_3 = 3}$$

$$-V_x - 5(I_2 - I_3) + V_x + 2I_3 = 0$$

$$\underline{-5I_2 + 7I_3 = 0}$$

rewrite


$$35I_2 - 20I_3 = 15$$

$$-35I_2 + 49I_3 = 0$$

$$29I_3 = 15 \quad I_3 = \frac{15}{29}$$

$$V_{out} = 2 \times \frac{15}{29} = \boxed{\frac{30}{29} \text{ Volts}}$$

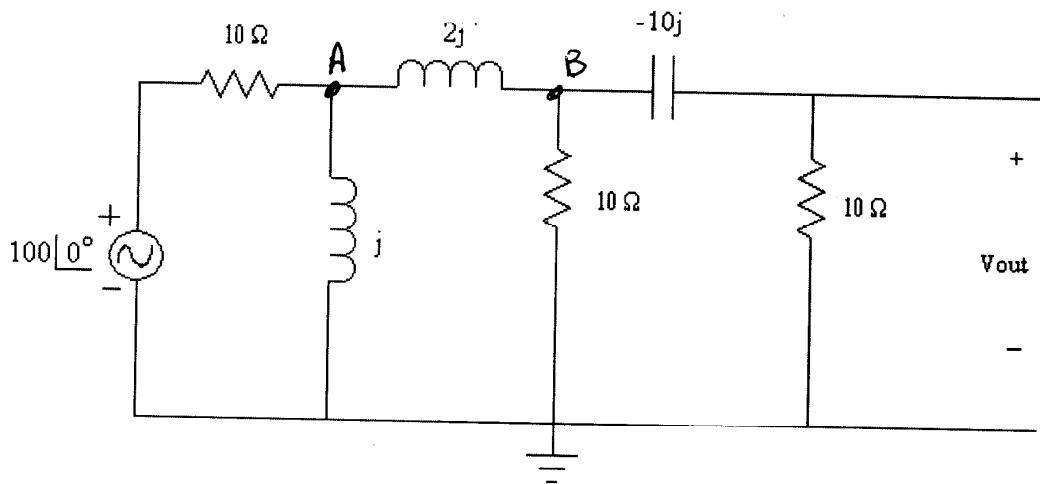4. (25 Points) Find V_{out} in the following circuit.



$$\rightarrow \frac{A-100}{10} + \frac{A}{j} + \frac{A-B}{2j} = 0 \quad A\left(\frac{1}{10} + \frac{1}{j} + \frac{1}{2j}\right) - B\left(\frac{1}{2j}\right) = 10$$

$$1: \underline{A(-1 - 1.5j) + B(0.5j) = 10}$$

$$\rightarrow \frac{B-A}{2j} + \frac{B}{10} + \frac{B}{10-10j} = 0 \quad A(0.5j) + B\left(\frac{1}{2j} + \frac{1}{10} + \frac{1}{10-10j}\right) = 0$$

$$\frac{1}{10-10j} \times \frac{10+10j}{10+10j} = \frac{10+10j}{200} = \frac{1}{20} + \frac{1}{20}j$$

$$A(0.5j) + B(-0.5j + 0.1 + 0.05 + 0.05j) = 0$$

$$2: \underline{A(0.5j) + B(-0.15 - 0.45j) = 0}$$

$$2' \quad A = \frac{B(0.45j - 0.15)}{0.5j} = B(0.9 + 0.3j)$$

$$1' \quad B(0.9 + 0.3j)(-1 - 1.5j) + B(0.5j) = 10$$

$$B[0.9 + 0.3j - 1.35j + 0.45 + 0.5j] = 10 \quad (6va)$$

$$B(1.54 - 0.82j) = 10$$

$$B = 5.6017 + 8.5062j$$


$$V_{out} = B \left(\frac{10}{10 - 10j} \right) = \frac{56.017 + 85.062j}{200} (10 + 10j)$$

$$= \frac{56.017 + 85.062j}{20} (1+j)$$


$$= \frac{56.017 + 85.062j + 56.017j - 85.062}{20}$$

$$= (-1.4523 + 7.0540j) V$$

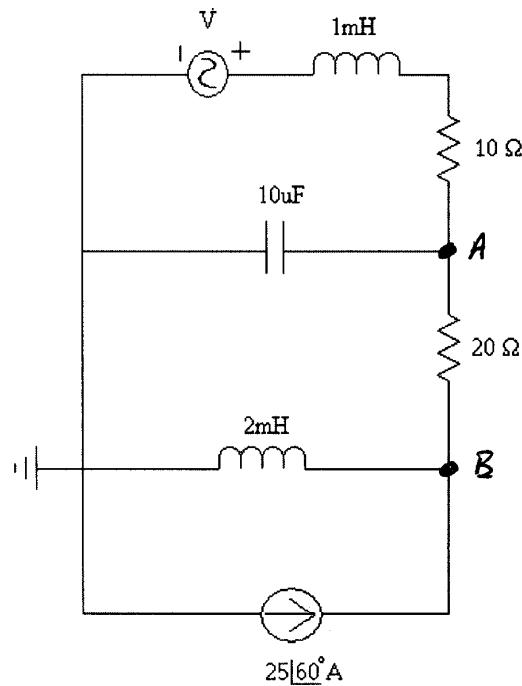5. (25 points) Find the power absorbed/supplied by each of the elements in the following circuit. Show that the powers sum to zero. $V = 1 \cos(100t+0)$ Volts.



rewire:

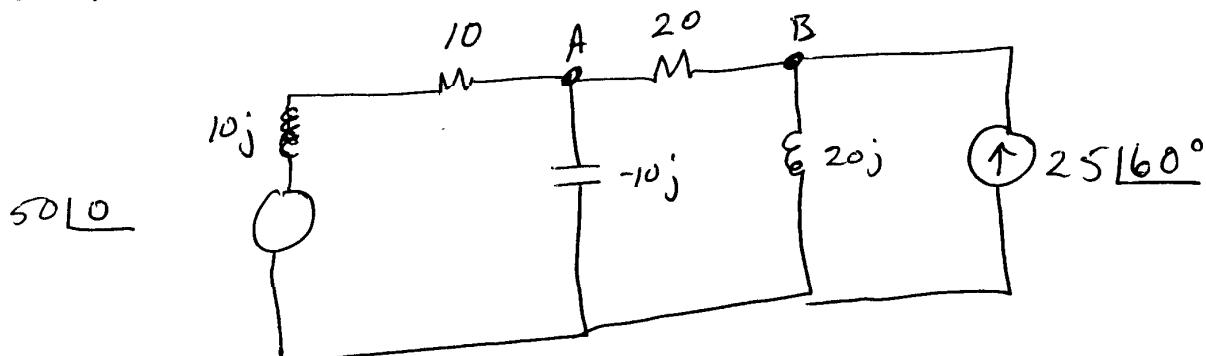

$$\frac{A-50}{10+10j} + \frac{A}{-10j} + \frac{A-B}{20} = 0 \quad \frac{B-A}{20} + \frac{B}{20j} = 2.5 \angle 60^\circ$$

over.

$$2' A\left(\frac{1}{20}\right) = -25 \underline{60^\circ} + B\left(\frac{1}{20} + \frac{1}{20j}\right)$$

$$A = B(1 + \frac{1}{j}) - 500 \underline{60^\circ}$$

$$A = B(1 - j) - 500 \underline{60^\circ}$$

$$1' A\left(\frac{1}{10+10j}\right) + A\left(\frac{-1}{10j}\right) + A\left(\frac{1}{20}\right) - \frac{B}{20} = \frac{50}{10+10j}$$

$$A\left(\frac{1}{10+10j} - \frac{1}{10j} + \frac{1}{20}\right) - \frac{B}{20} = \frac{50}{10+10j}$$

$$A\left(\frac{10-10j}{200} + .1j + .05\right) - \frac{B}{20} = \frac{50(10-10j)}{200}$$

$$A(.1 + .05j) - B(.05) = 2.5 - 2.5j$$

$$B(1-j)(.1 + .05j) - B(.05) = 2.5 - 2.5j + 500 \underline{60^\circ} (.1 + .05j)$$

$$B = 10.359 + 35.9808j = 37.4423 \underline{73.9387^\circ}$$

$$A = B(1-j) - 50 \underline{60^\circ} = 21.3397 - j 17.67951$$

Powers: C2: $\frac{1}{2} I_m V_m \cos(\theta_V - \theta_Z) = 45.4247 W$


$$I_{20n} = \frac{B-A}{20} = 2.7386 \underline{101.5651} \quad P = \frac{1}{2} \cdot 2.7386^2 20 = 74.9993 W$$

$$I_{Vn} = \frac{B-A}{10j} = 2.3811 \underline{166.6690^\circ} \quad P = \frac{1}{2} \cdot 2.3811^2 10 = 28.34132 W$$


$$I_{Vs} = \frac{1}{2} I_m V_m \cos(\theta_V - \theta_Z) = \left(\frac{1}{2}\right)(2.3811)(50) \cos(-166.6690^\circ) \\ = -57.92355 W$$

6. (10 points) Consider the two circuits shown below.

A)

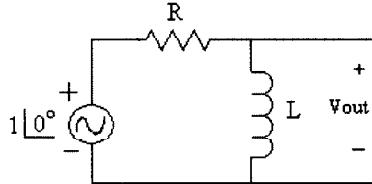

B)

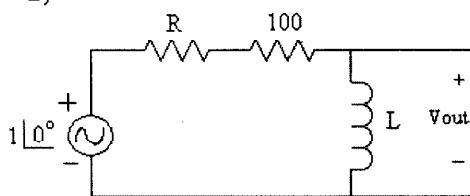

When $\omega=58,000$ rad/sec, the output of circuit A is found to be $0.5017\angle59.8863^\circ$. The output of circuit B at $\omega=58,000$ rad/sec is found to be $0.4664\angle62.1985^\circ$.

Find the values of R and L.

$$\begin{aligned}
 V_{outA} &= \frac{j\omega L}{R + j\omega L} 1\angle 0^\circ \quad \cancel{V_{outA}} = \\
 &= \frac{j\omega L (R - j\omega L)}{\omega^2 + \omega^2 L^2} = j\omega L R + \omega^2 L^2 \\
 &\Rightarrow V_{outA} = \tan^{-1} \left(\frac{\omega L R}{\omega^2 L^2} \right) \\
 &= \tan^{-1} \left(\frac{R}{\omega L} \right)
 \end{aligned}$$

$$\text{Similarly, } \cancel{V_{outB}} = \tan^{-1} \left(\frac{R + 100}{\omega L} \right)$$

$$\therefore \tan^{-1} \left(\frac{R}{58000 L} \right) = 59.8863^\circ \quad \tan^{-1} \left(\frac{R + 100}{58000 L} \right) = 62.1985^\circ$$

$$\begin{aligned}
 \Rightarrow R &= 1000 \Omega \\
 L &= .01 \text{ H}
 \end{aligned}$$